

Bandstop filters and

Gian Laager and Sebastian Rast

April 6, 2023

1 Introduction

1.1 Goal

1.2 Hypothesis

A LC circuit has the ability to oscillate on its own i.e. it can produce a current that looks like some kind of sin-wave over time. This feature is provided by the interaction of a coil and a capacitor. The circuit has to be assembled according to the circuit in fig. 1.

1.3 How does a LC circuit work?

2 Theoretical Background

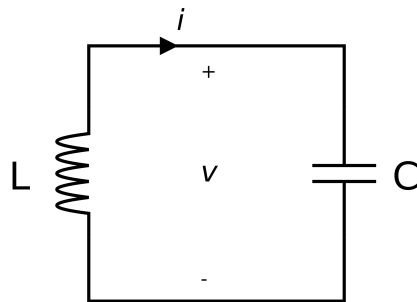


Figure 1: Schematic of a LC circuit

In principle a LC circuit works as following:

- I. At the beginning the capacitor is charged and a voltage can be measured over the capacitor. All the energy is stored in the capacitor.
- II. Because of the voltage, current flows from the capacitor to the inductor and the inductor is charged.

- III. The charging of the inductor leads to a magnetic field produced by the coil. According to the Lenz rule this magnetic field acts against the flowing current. Thus the increase of the current happens slowly at the beginning. At the end though, the current increases with the magnetic field until a maximum is reached. At this time the capacitor is fully discharged and the energy is stored in the inductor.
- IV. After the current has reached its maximum it will slowly decrease and the magnetic field is dissipated. Hence no voltage is applied to the inductor.
- V. The same cycle starts again just with a negative voltage.
- VI. The current flows on and charges the capacitor until all of the energy is transferred to the capacitor.

2.1 Bandstop filter

A bandstop filter has the ability to pass almost all frequencies but filter very specific frequencies (= bands) (see fig.2). Bandstop filters are used in various applications as for example guitar amplifiers or the Raman spectroscopy.

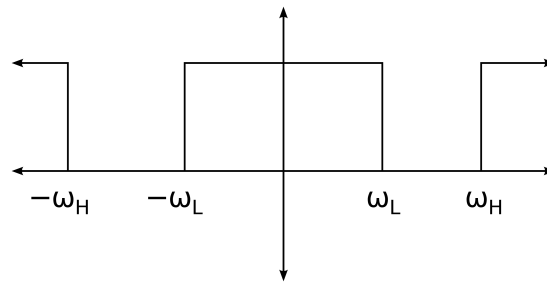


Figure 2: Fourier Transformation of the angular frequency spectrum of a bandstop filter.

3 Experimental arrangement

The following materials are necessary to conduct the experiment:

- oscilloscope that can generate waves
- breadboard and jumper cables
- 1k Ω , 200 Ω , 10k Ω resistors
- 100 μ F, 220 μ F, 47 μ F capacitors

- cables to connect the oscilloscope to the circuit
- one 6H inductor

The circuit has to be assembled according to the following schematic (fig. ??). We did different measurements with the different electrical components from above.

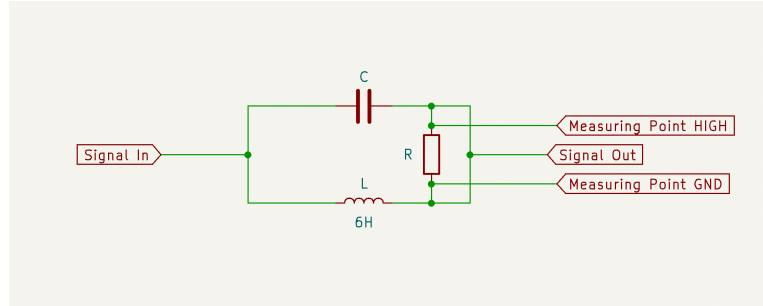


Figure 3: Schematic

We conducted an impulse response analysis. With this type of analysis one sends a very short electrical pulse through a system and watches how the system reacts to this signal. In LC-circuits the short electrical pulse leads to the charging of the capacitor and thus to a oscillating circuit. The oscillation is damped by a resistor so that the oscillation stops until the next pulse arrives.

3.1 Measurement process

4 Analysis

4.1 Observations

We could observe strange behaviour when the Measuring Point GND (see fig. ??) was not connected to the circuit. The measured signal oscillated way more than when the pin was connectd.

4.2 Error discussion

5 Conclusion